

ELEC402 Assignment4 – NAND3 Simulation and Layout


Eric Wu 75286914

1. NAND3 Simulation & Layout

Area/delay:

Area	Delay (tphl)	Delay (tplh)	Area x Delay(ave)
$0.22464\mu m^2$	17.036ps	13.71ps	$3.453\mu m^2ps$


Layout + DRC results:

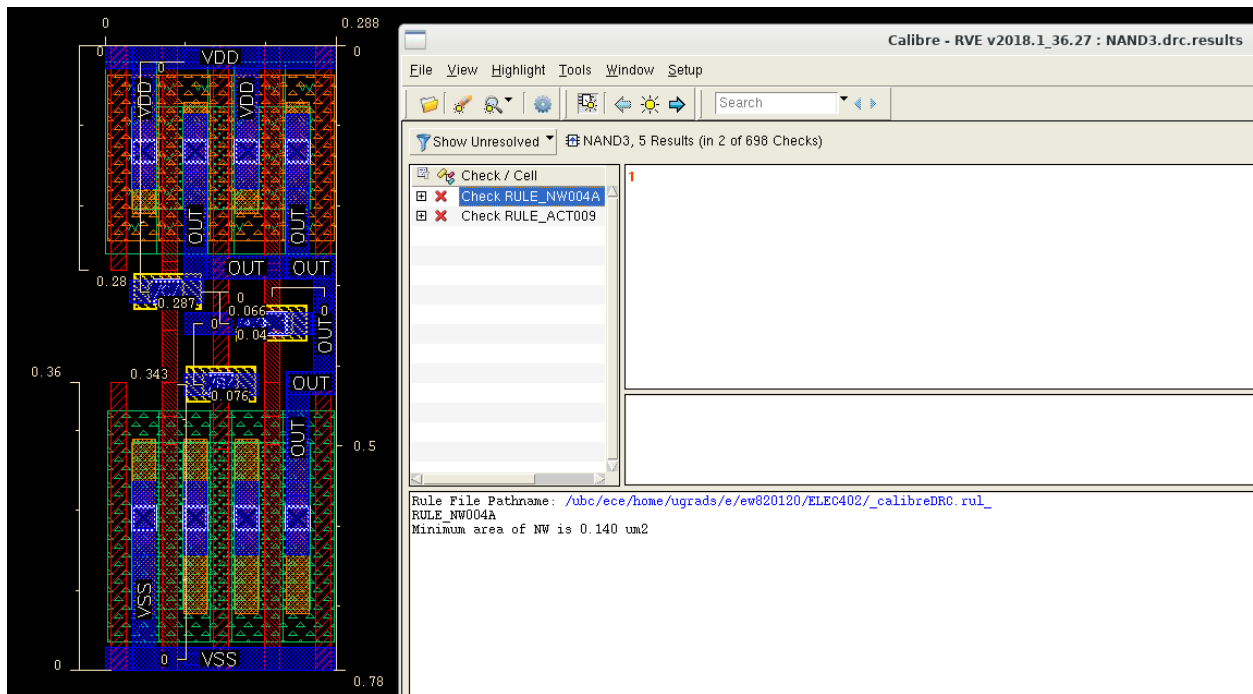

To get equal tphl and tplh, PMOS fins were set to 4 and NMOS fins were set to 6.

The width was $0.28\mu m$ and $0.36\mu m$ respectively.

Schematic for LVS:

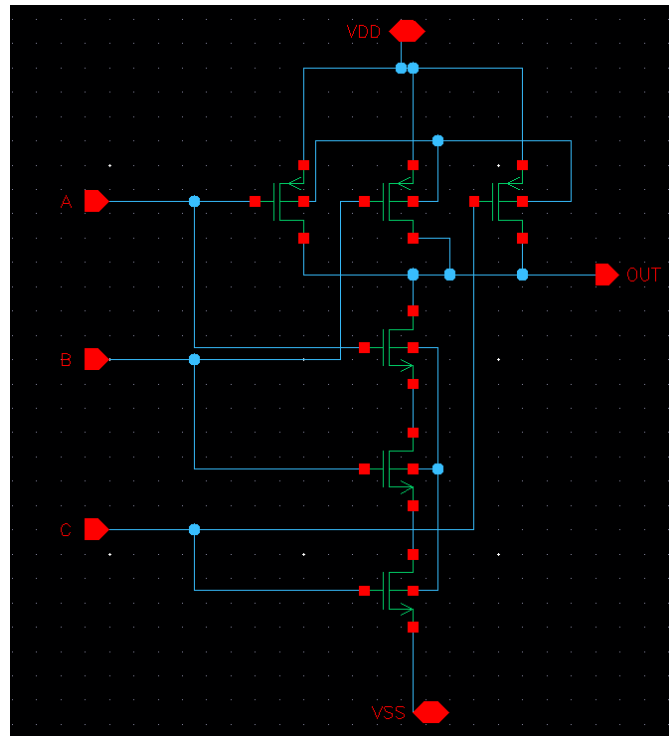

LVS results:

Calibre - RVE v2018.1_36.27 : svdb NAND3

File View Highlight Tools Window Setup Help

Search

Navigator

Results

- Extraction Results
- Comparison Results

Reports

- Extraction Report
- LVS Report

Rules

- Rules File

View

- Info
- Finder
- Schematics

Setup

- Options

Extraction Results

Layout Cell / Type	Source Cell	Nets	Instances	Ports
NAND3	NAND3	8L, 8S	1L, 1S	6L, 6S

Cell NAND3 Summary (Clean)

```
#####  
#          #          #          #          #  
#          #          #          #          #  
#          #          #          #          #  
#          #          #          #          #  
#          #          #          #          #  
#####
```

LAYOUT CELL NAME: NAND3
SOURCE CELL NAME: NAND3

INITIAL NUMBERS OF OBJECTS

	Layout	Source	Component Type
Ports:	6	6	
Nets:	10	10	
Instances:	3	3	NI (4 pins)
	3	3	MP (4 pins)
Total Inst:	6	6	


PEX Netlist File - NAND3.pex.netlist

```
PEX Netlist File - NAND3.pex.netlist
File Edit Options Windows

* VDD VDD
* A A
* B B
* VSS VSS
* C C

NM4 NET1 B NET2 NET6 NETET L=2e-08 W=2.08e-07 NFIN=6 ADEJ=2.112e-15
+ ASEJ=2.112e-15 PDEJ=5.76e-07 PSEJ=5.76e-07
NM5 NET2 C N VSS NM5+ NET6 NETET L=2e-08 W=2.08e-07 NFIN=6 ADEJ=1.056e-15
+ ASEJ=9.12e-16 PDEJ=2.64e-07 PSEJ=2.28e-07
NM3 N OUT NM3 d A NET1 NET6 NETET L=2e-08 W=2.08e-07 NFIN=6 ADEJ=1.824e-15
+ ASEJ=1.056e-15 PDEJ=5.04e-07 PSEJ=2.64e-07
NM1 N OUT MM2 d B N VDD MM1+ NET3 PEET L=2e-08 W=1.28e-07 NFIN=4 ADEJ=1.408e-15
+ ASEJ=1.408e-15 PDEJ=3.84e-07 PSEJ=3.84e-07
NM2 N OUT MM2 d C N VDD MM1+ NET3 PEET L=2e-08 W=1.28e-07 NFIN=4 ADEJ=7.04e-16
+ ASEJ=7.04e-16 PDEJ=3.36e-07 PSEJ=1.76e-07
MM0 N OUT MM0 d A N VDD MM1+ NET3 PEET L=2e-08 W=1.28e-07 NFIN=4 ADEJ=2.112e-15
+ ASEJ=7.04e-16 PDEJ=3.36e-07 PSEJ=1.76e-07
C 8 C VSS O 0219681f
C 17 NET2 VSS O 023649f
C 22 B VSS O 0266234f
C 29 A VSS O 0203244f
C 34 NET1 VSS O 023643f
*
#include "NAND3.pex.netlist NAND3.pxi"
*
.ends
*
```

1	2	3	524	5
---	---	---	---	---	---	---	---	---	----	----	----	----	-----	-----	-----	-----	---

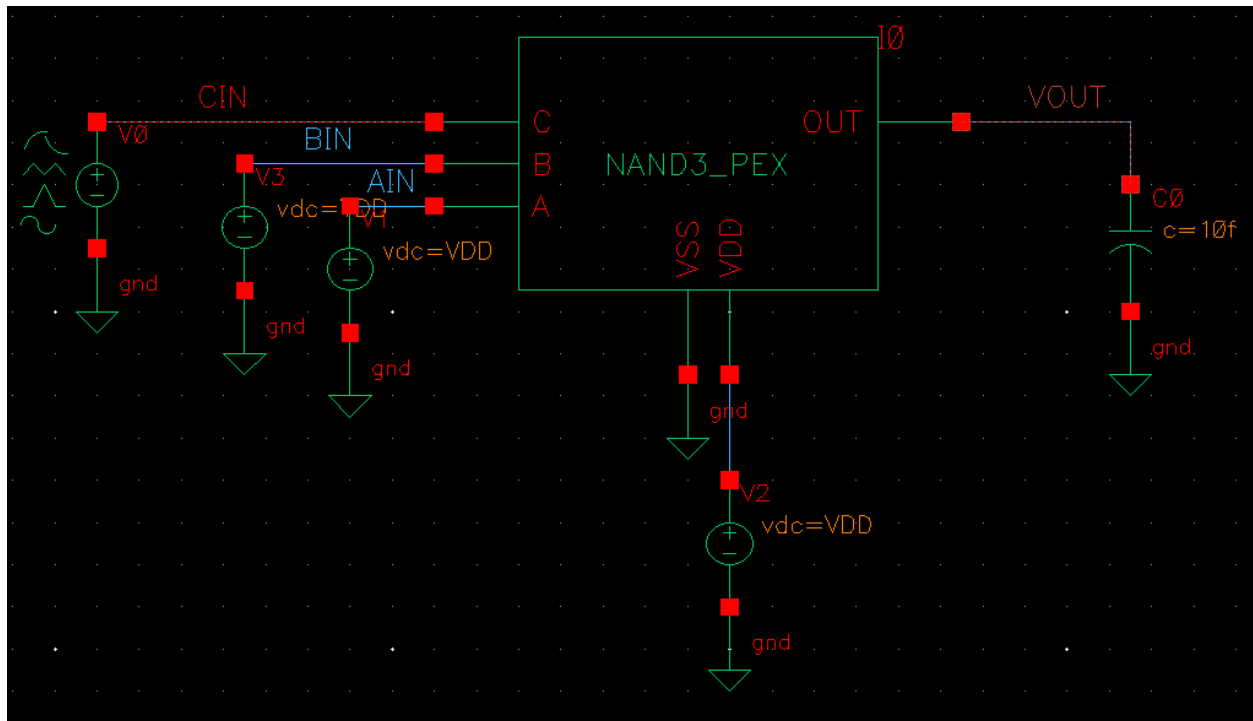


For the pull up network, this transition would only connect one path giving us the WC tpb

For the pull down network, the capacitance in A, B would be charged before the transition and

We will measure `tpll` and `tplh` using the above testbench (toggling `C` between high and low)

WV:

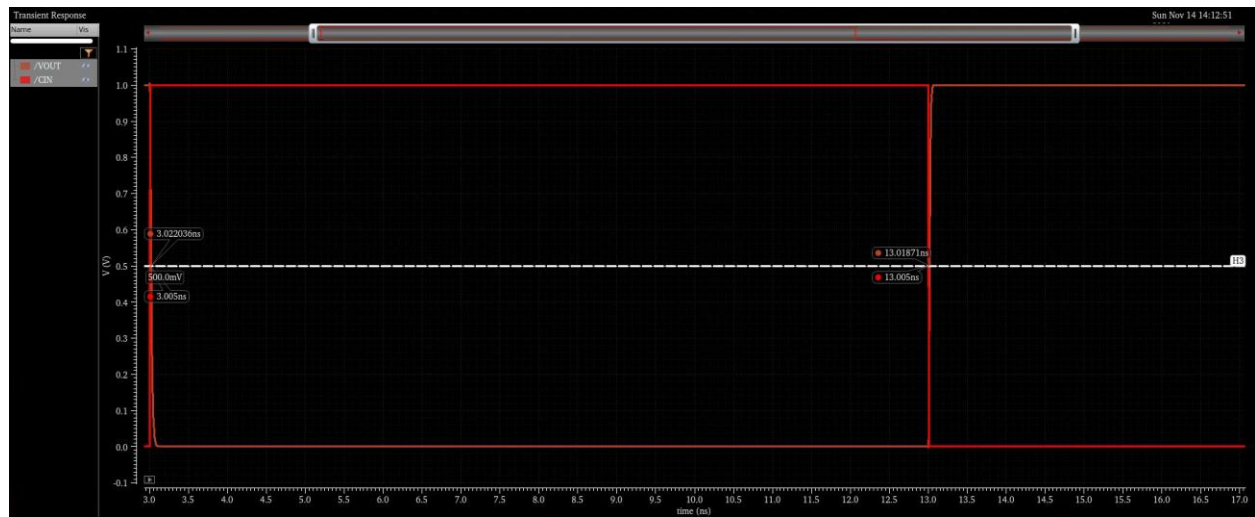

$t_{phl} = 17.036\text{ps}$, $t_{plh} = 13.71\text{ps}$.

The difference is $= 3.326\text{ps}$, which fulfills the requirement $< 5\text{ps}$ difference.


2.

2.

logic function

$$\overline{Y} = (A+B)CD, Y = (\overline{A}\overline{B}) + \overline{C} + \overline{D}$$

(a) sizing

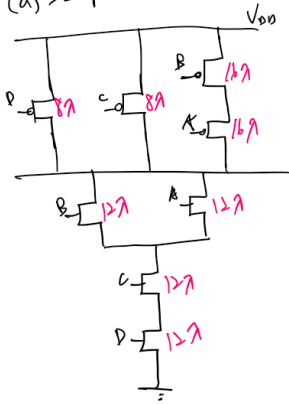

WC_{pu} = only AB branch

WC_{pd} = ACD or BCD

(b)

Worst case t_{PHL}:

WC transition would be when parallel transistors only have one path that's conducting.

⇒ ABCD → ABCD would be the WC transition because if D was originally 0110 → 0111

opp, all the other nodes would have to discharge after the transition.


Worst case t_{PLH}:

Using the same logic as above:


WC transition: ABCD → 0011

This is the case that the most nodes will have to charge.

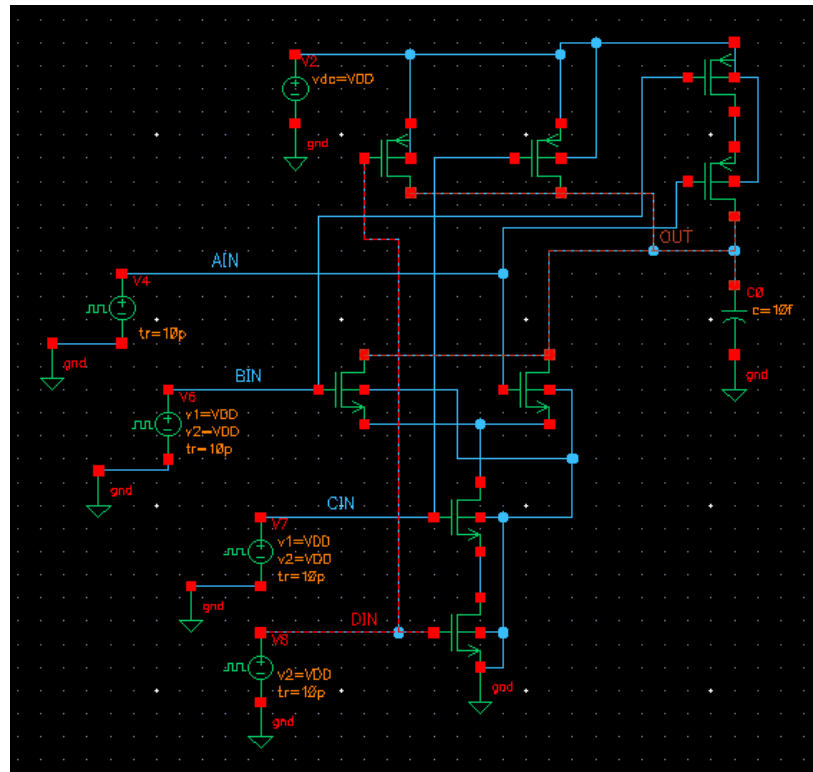Tphl test bench schematic (sizing was achieved using $2\lambda = 1 \text{ fin}$):




Tphl WV results:

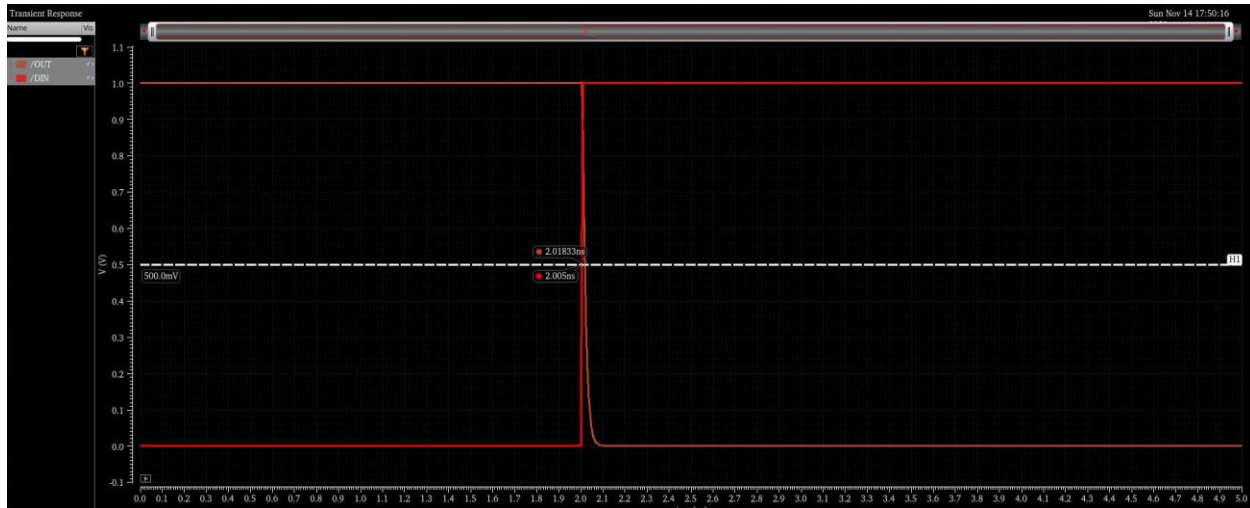


From the results waveform, we can see that the tphl is 13.33ps.

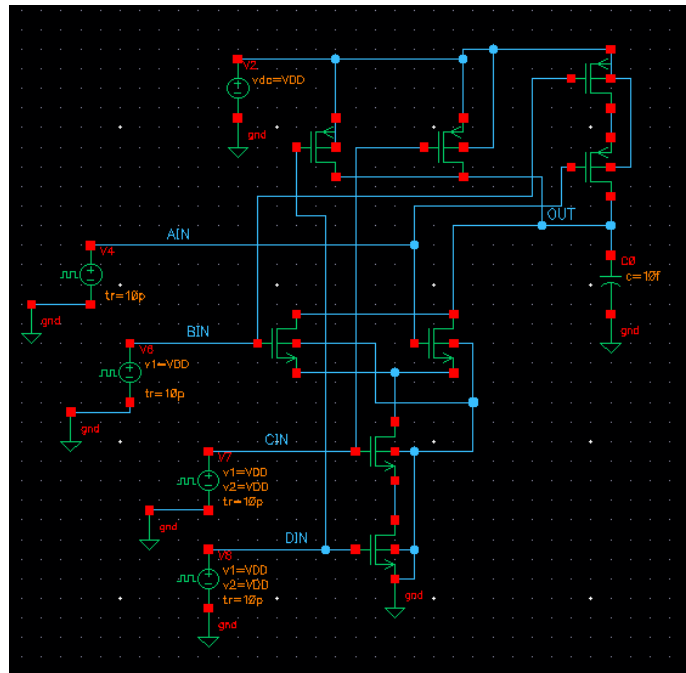Tplh testbench schematics (sizing was achieved using $2\lambda = 1 \text{ fin}$):



Tplh WV results:

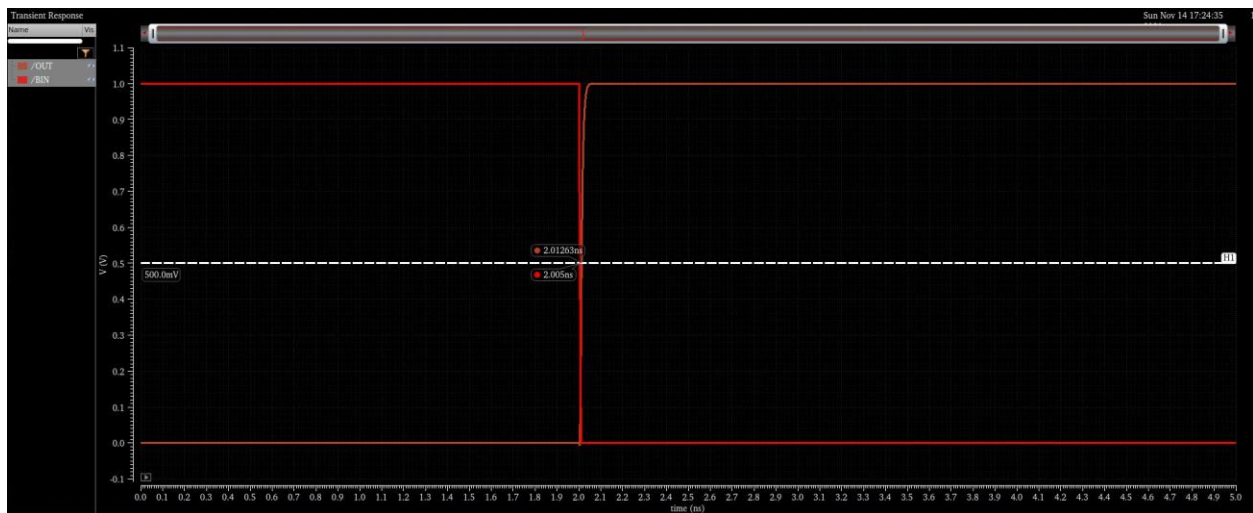


From the results waveform, we can see that the tplh is 7.63ps.

3.


3(a)

$$\overline{OUT} = C = \overline{A}(sel + sel\overline{B}) + \overline{B}(sel + sel\overline{A})$$
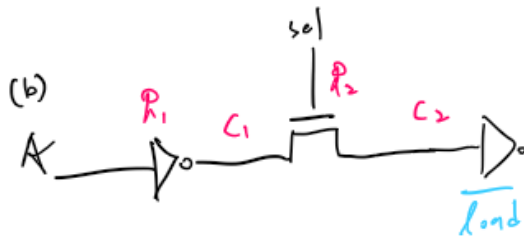
$$OUT = \overline{\overline{A}(sel + sel\overline{B}) \overline{B}(sel + sel\overline{A})} = (A + (\overline{sel} \overline{sel\overline{B}})) (B + (sel \overline{sel\overline{A}}))$$



↓ eq circuit

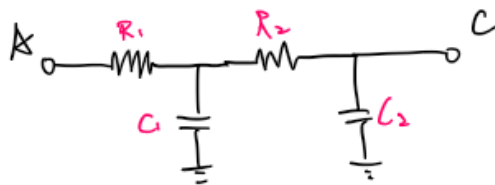

$$R_1 = R_{eqn} \times \frac{L}{W} = 12.5k \times \frac{1}{2} = 6.25k \Omega$$


$$R_2 = R_{eqn} \times \frac{L}{W} = 6.25k \Omega$$

$$C_1 = 12n \times C_{eff} + \underbrace{2 \times 4n \times C_{eff} + 4n \times C_g}_{\text{MOS ON (sel = high)}} = 2.4 fF$$

$$C_2 = \underbrace{8n \times C_{eff} + 4n \times C_g}_{\text{MOS ON}} + 12n \times C_g \times f = 1.6 fF + 2.4 fF$$

(c)
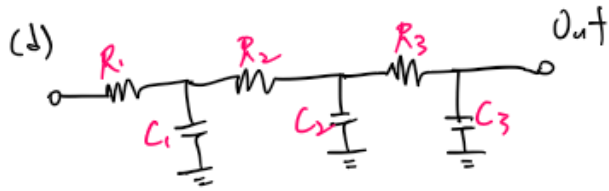
$$\tau = R_1 C_1 + (R_1 + R_2) C_2 = 35ps + 30ps$$



$$R_3 = \frac{6.25k}{f}, \quad C_3 = 1.2f \text{ fF} + \underbrace{50 \text{ fF}}_{\text{load}}$$

$$RC \text{ delay} : (R_1 C_1 + R_2 C_2 + R_3 C_3)$$

$$= (15 \text{ ps} + (10 \text{ ps} + 15f \text{ ps})) + (1.5 \text{ ps} + \frac{312.5}{f} \text{ ps})$$

$$= 32.5 \text{ ps} + (15f + \frac{312.5}{f}) \text{ ps}$$

(e) To get smallest delay: minimize $(15f + \frac{312.5}{f})$

$$\frac{d(15f + \frac{312.5}{f})}{df} = 0 \Rightarrow \underline{\underline{f \approx 4.56}}$$

$$\left. \frac{d(15f + \frac{312.5}{f})}{df^2} \right|_{f=4.56} > 0 \Rightarrow \text{local min}$$